
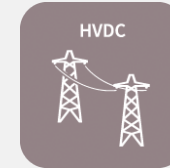


78 W Auxiliary power supply for 22 KW drive using Infineon 1700 V SiC MOSFET


Simon SHI
Infineon Technologies, Shenzhen

CoolSiC™ MOSFET 1700 V discrete

Auxiliary power supply for:

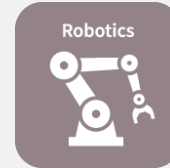

...


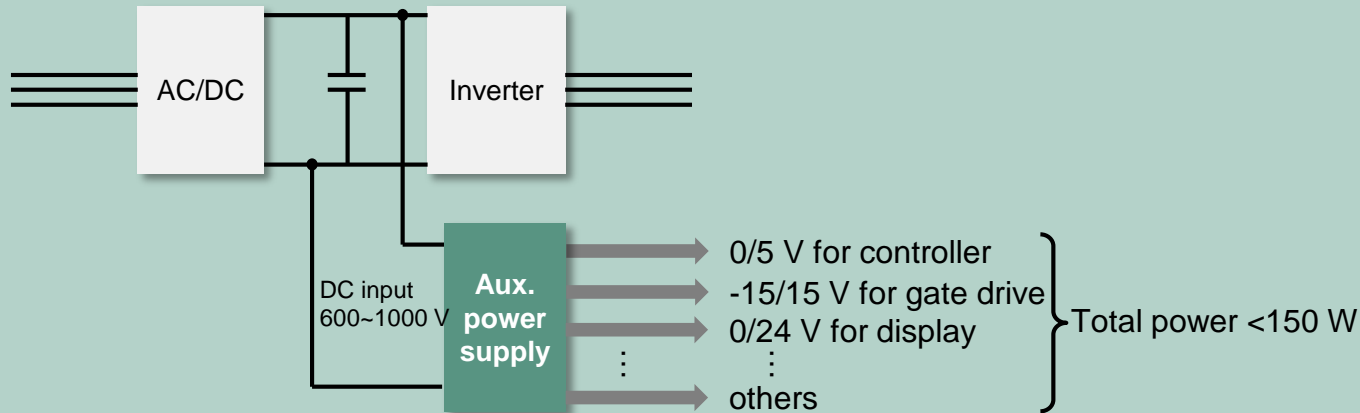


1700 V SiC MOSFET meets the preferred industry practice in low-power auxiliary circuits


preferred

reality with silicon devices

1700 V SiC simplicity

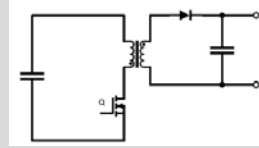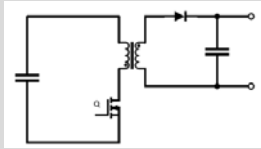



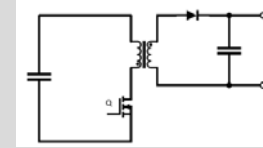
Low efficiency and challenges with V_{DS} derating margin limit the use



Simple converter

but needs a high V_{DSS} low-loss device

V_{DS} derating margin $> 10\%$

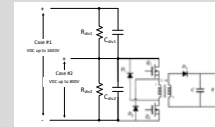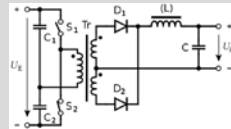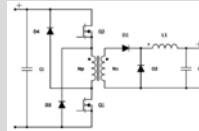

Complex work-around designs for efficiency, V_{DS} derating margin limits the use to $V_{DC} \leq 800$ V systems


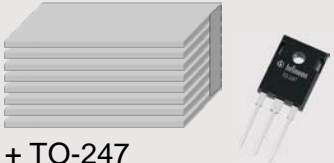

Simple converter at high efficiency

Up to V_{DC} 1000 V systems

V_{DS} derating margin up to 15%




Enabled by 2.5% higher efficiency vs. silicon - SMD package simplifies the main switch assembly


DC/DC flyback converter	Main switch assembly	Remarks
Single-switch in SMD	 TO-263-7 extended creepage version	SMD soldering, thermal vias in PCB
Single-switch in TO-247	 Heatsink + TO-247	THD needs heatsink
Two-switch in TO-247	 Heatsink + 2 pcs TO-247 + 2 pcs TIM	Needs two TIM and a heatsink

... but it needs a bit more than putting a SiC MOSFET into a SMD package

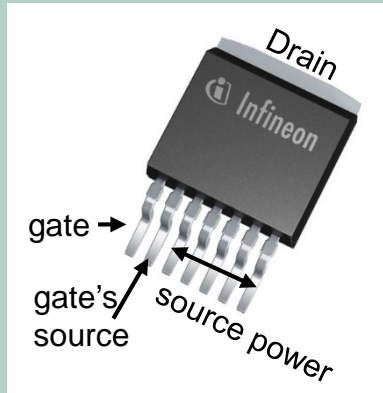The new Infineon D²PAK 7L package Special designed packages for each voltage class




1700 V package

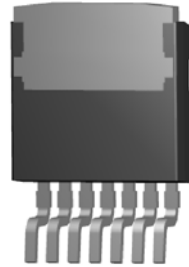

Creepage: >7.1 mm


Clearance: >7.1 mm

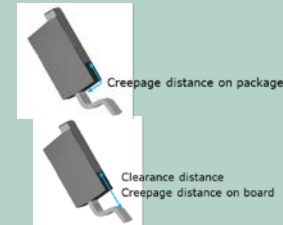

- › Dedicated technology to enable reflow soldering w/o delamination between chip and mold
- › New die attached compensating for the higher R_{th} usually being in place in SMD packages vs. THD
- › Chip technology with new gate control conditions

Optimized gate voltage for direct drive from controller

Typical fly-back controller	Output gate voltage
NCP1207	Change with V_{cc}
NCP1339	0/12 V
NCP1379	0/13 V
FAN604H	0/14.5 V
L6565	$0/V_{cc} - 2$ V
UCC28600	0/13 V
UCC28C44	Change with V_{cc}
LM5023	0/12.9 V

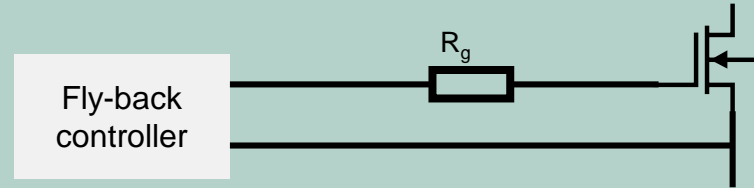

Perfectly fitting gate voltage

SiC MOSFETs	Recommended gate voltage
CoolSiC™	0/12~15 V

Infineon's CoolSiC™ MOSFET 1700 V is the SiC MOSFET that could be directly driven by most fly-back controllers

The game changing technology in reality

CoolSiC™
with quasi-resonant controller






CoolSiC™
with fixed frequency controller




- › Ultra low switching loss of CoolSiC™ MOSFET 1700 V discrete:
 - Natural convection cooled
 - SMD soldered directly on the PCB
 - Operated directly from flyback controller


Functional test result

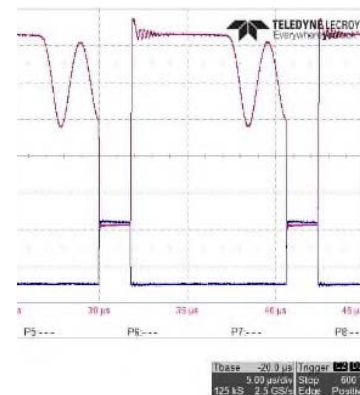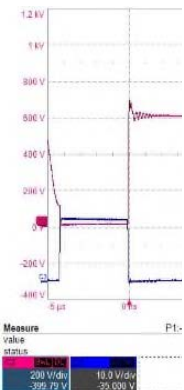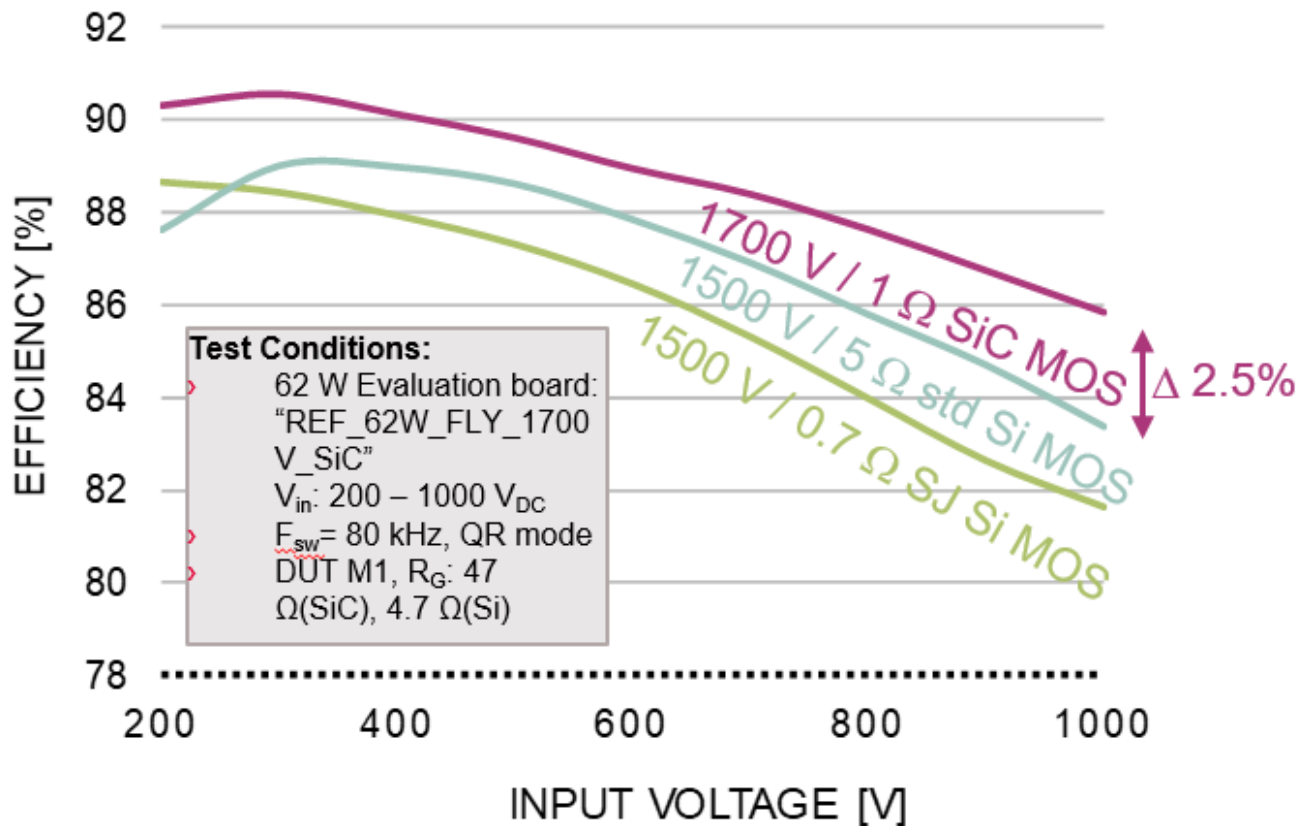

Thermal consideration

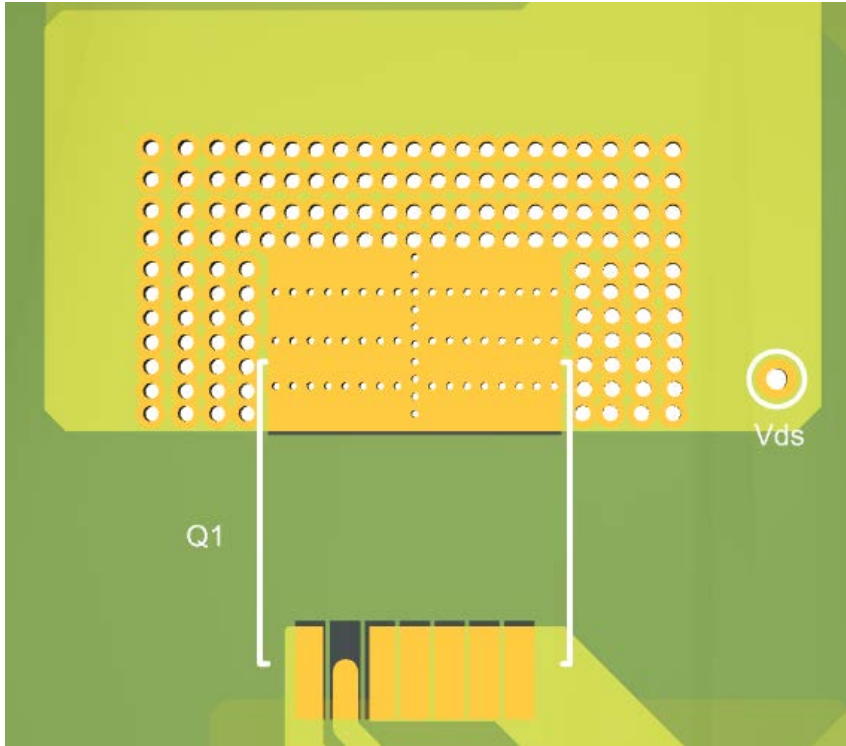

Reinforced insulation for transformer

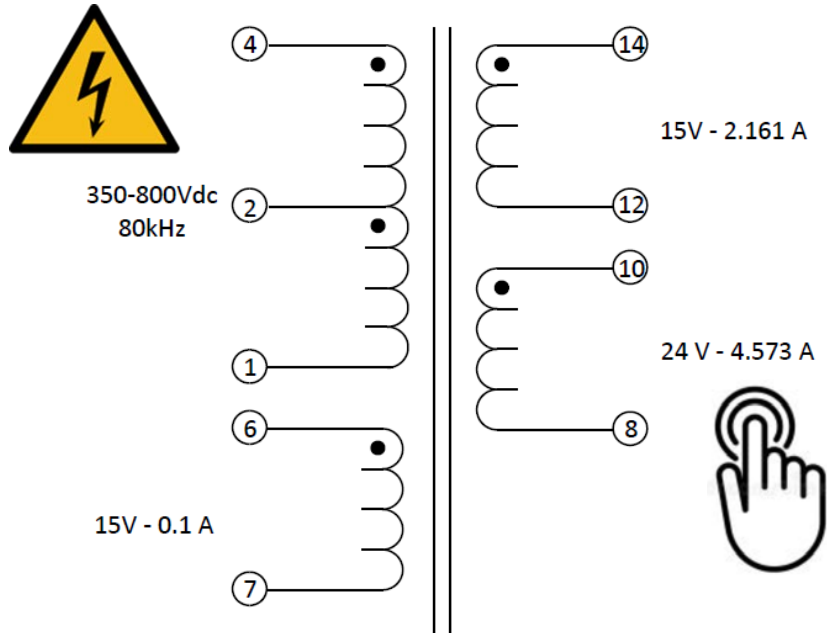

Increase the physical distance between primary - secondary windings.




Fully insulated wire

Remove voids in the transformer


Change the material with higher CTI

PD test – IEC 60664-1

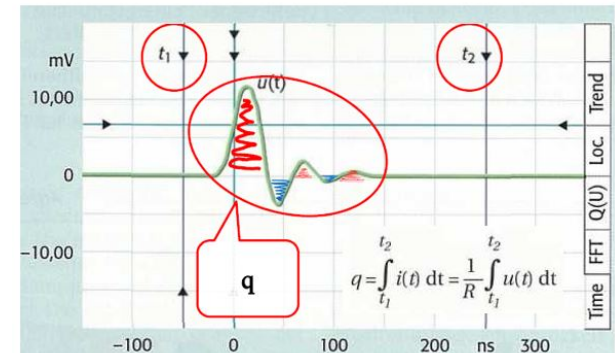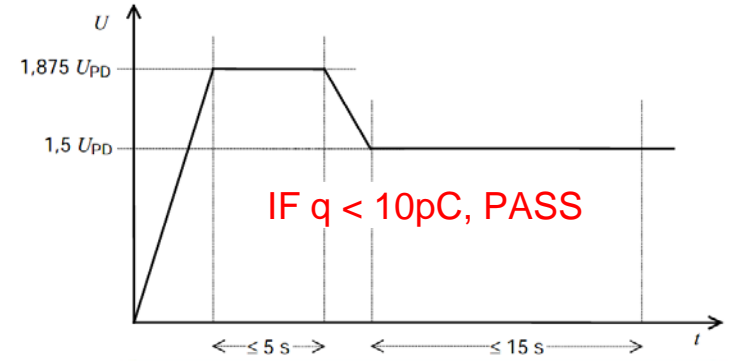
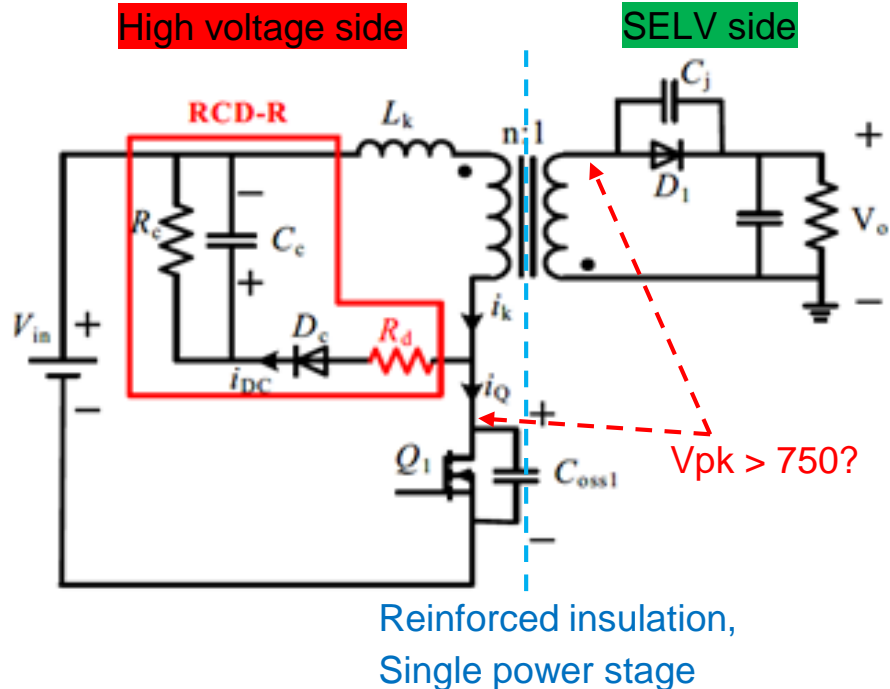
if the recurring peak working voltage across the insulation is greater than 750 V and the voltage stress on the insulation is greater than 1 kV/mm, PD test is mandatory.



Transformer optimization and PD result

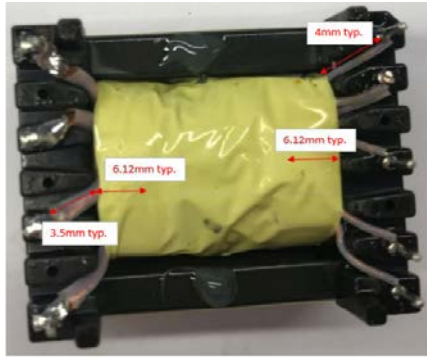


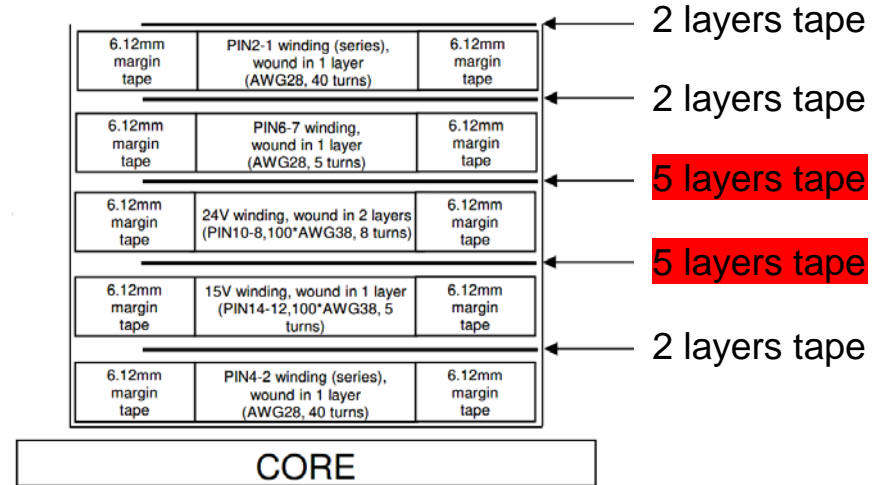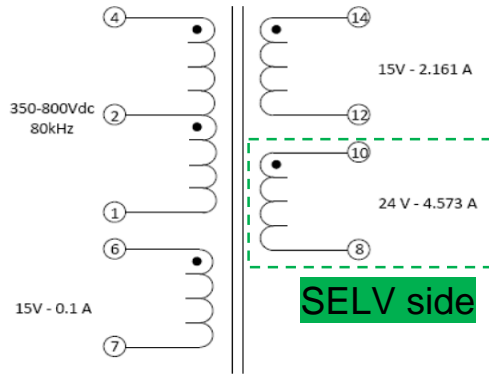- › Increase creepage distance between high voltage winding and SELV winding to 12.24mm
- › Increase thickness of insulation tape
- › Replace transformer bobbin material with CTI 1 material




Sample #2 Pass Average PD= 3.36pC Max PD= 9.36pC Average Voltage= .675806 kV
 Sample #2 Manual Mode Max Inception 1.23kV Max Extinction 1.07kV

Summary

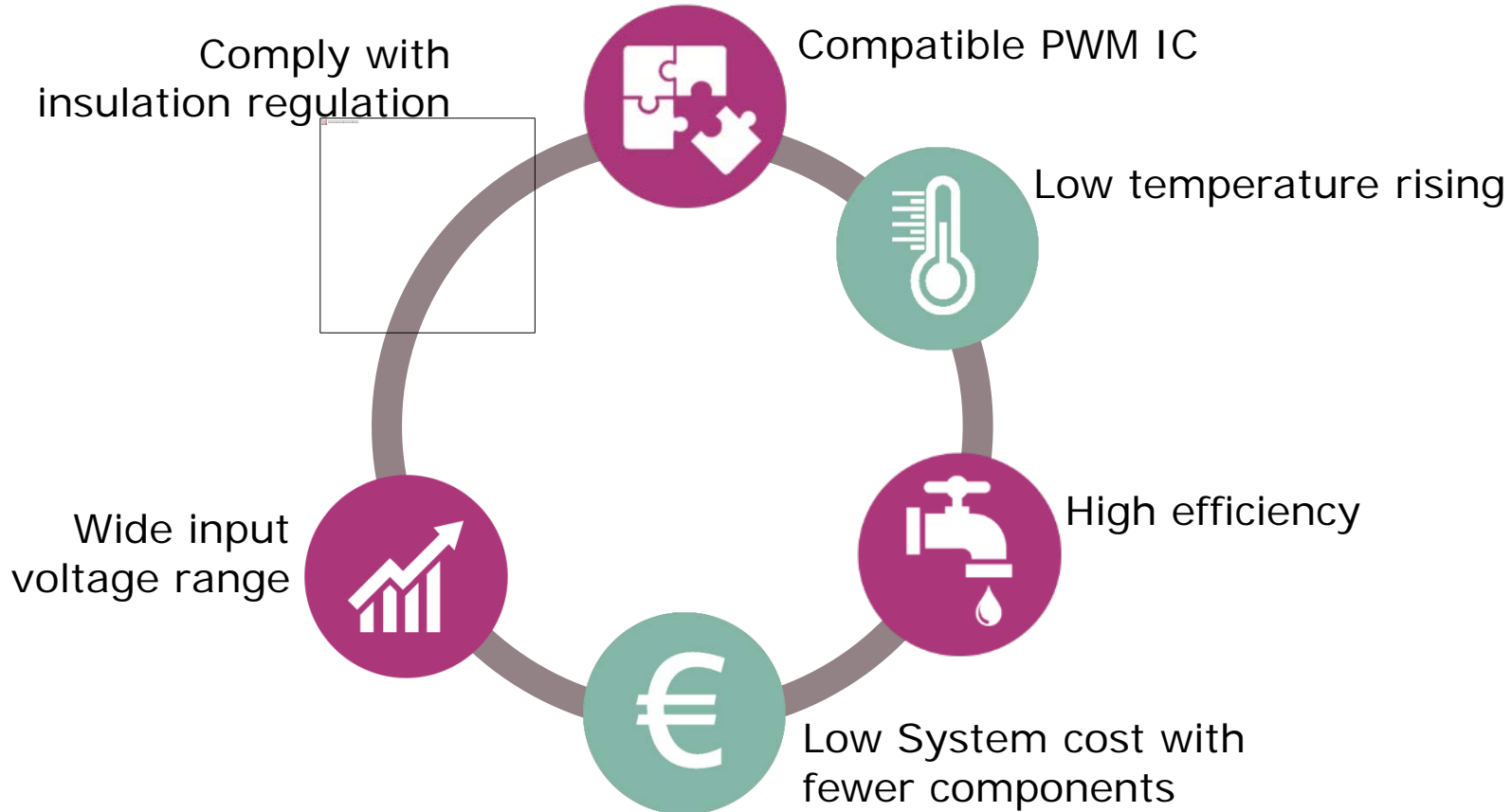


CoolSiC™ - a revolution to rely on!

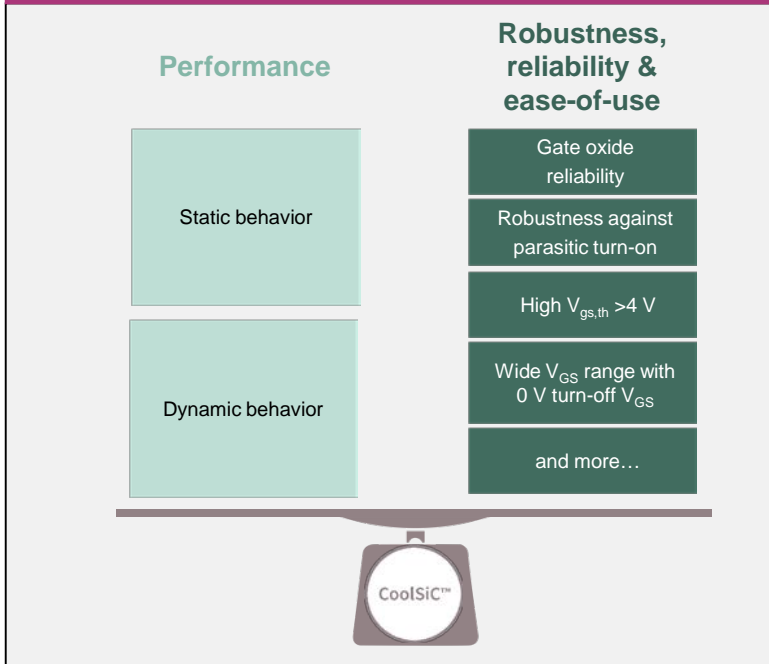Striving for a SiCMOS technology with optimal balance between performance and robustness ...



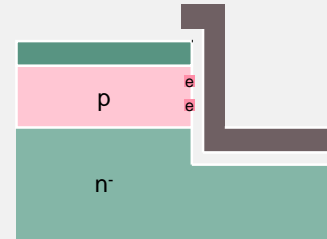... has led Infineon to choose a trench based structure for our CoolSiC™



Infineon trench technology


- > Superior **gate oxide reliability**
- > Allows for an **effective screening of defects**
- > Ideally suited for further **Ron x A reduction** in future
- > Enables flexible parameter set for **application-specific products**
- > **Industry is gradually moving to trench**

1700 V SiC MOSFET is new addition in Infineon's CoolSiC™ portfolio


SiC MOSFETs	TO-247-4	TO-247-3	D ² PAK-7
650 V	27,48,72,107 mΩ	27,48,72,107 mΩ	1200 V 1700 V ext. creepage
1200 V	30, 45, 60,90, 140, 220, 350 mΩ	30, 45, 60,90, 140, 220, 350 mΩ	30, 45, 60,90, 140, 220, 350 mΩ ¹
1700 V	New		450, 650, 1000 mΩ

SiC Schottky diodes	TO-220 R2L	DDPAK	TO-247-3	TO-247	D ² PAK R2L	ThinPAK 8x8	TO-247 dual die	DPAK R2L
650 V	2,-20 A	2,4,6,8,10,12,16, 20 A	10,12,16, 20, 30, 40 A	10,12,16,20, 30, 40 A	2,3,4,5,6,8,9,10,1 2 A	2,4,6,8,10, 12 A	20,24,32, 40 A	3,4,5,6,8,9,10,12 A
1200 V	2,5,8,10,16,20 A			10,15,20,30,40 A				2,4,8,10 A

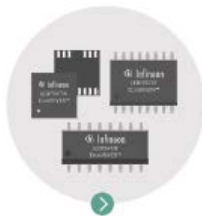
Orange: also available in automotive grade products



Gate drivers IC

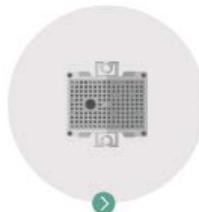

Modules

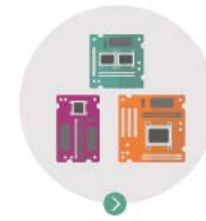

Evaluation boards

Contact



Name: Simon SHI

Email address:
simon.shi@infineon.com





Part of your life. Part of tomorrow.

